

**BANGALORE INSTITUTE OF TECHNOLOGY**  
**K R ROAD, V V PURA, BENGALURU-04**  
**DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING**  
**I Internals - 2024-25 (Odd)-Improvement**

**BATCH: 2023**

**COURSE (CODE):**

**SEM: 3<sup>rd</sup>**

**DATE & TIME:** / /2024 ,3:30PM to 4:30PM

**MAX MARKS: 30**

**USN:**

**Note: Answer any one full question from each PART**

Q. No.	PART A (Module – I, III)	15M	CO's	PO's	Blooms Levels
1. a)	<b>Find</b> the minimum product of sum for given function using K-map and also identify the essential prime implicants. $F(a,b,c,d)=m_6+d_4+m_7+m_{12}+d_{11}+m_{13}+m_1+m_{15}$ and Realize the simplified circuits using basic gates.	5	1	1,2,3	3
1.b)	<b>Prove</b> that dual theorem $x+x=x$ and $x.x=x$	5	1	1,2,3	3
1.c)	With neat diagram explain basic functional units of computer.	5	3	1,2	2
	<b>OR</b>				
2.a)	i)Solve the sum of product for given function using K-map and find all essential prime implicants . $X(p,q,r,s)=\pi M(6,7,10,12,13)+d(0,4,8,11)$ ii) Obtain the sum of product for given Boolean expression using k-map $F= A'B'+BD+CD+B'C'$ .	4	1	1,2,3	3
2.b)	Write a short note on parallelism .	6	3	1,2,3	2
2.c)	Find the complement of the functions a) $F_1 = x'yz' + x'y'z$ and b) $F_2 = x(y'z' + yz)$ .	5	3	1,2,3	2
	<b>PART B(Module –I, III)</b>	<b>15M</b>			
3.a)	Explain pipeline and super scalar operation , CISC and RISC operation.	5	1	3	3
3.b)	Implement the Boolean function with OR and INVERTER gates only. $F = xz + x'z' + x'y$	4	1	3	3
3.c)	Using the basic theorems and postulates of Boolean algebra, simplify the following Boolean expression: $F = x'y'z + xyz + x'y'z + x'y'z$ .	6	1	1,2,3	3
	<b>OR</b>				
4.a)	Implement EX-NOR gate using universal NAND Gate.	5	1	1,2	3
4.b)	Write the VHDL program for Full adder.	4	1	1,2,5	3
4.c)	Explain the different registers in the computer .	6	3	1	2